



Name:

Index:

Reg. No.:

Class:

Date:

Chapter 10

Boolean Logic

Logic Gates


What is Boolean logic?

- Boolean logic is used in computer science and electronics to make **logical decisions**
- Boolean operators are either **TRUE** or **FALSE**, often represented as **1** or **0**
- Inputs and outputs are given **letters to represent them**
- To define Boolean logic we use **special symbols** to make **writing expressions** much **easier**


What are logic gates?

- Logic gates are a **visual way** of representing a **Boolean expression**
- The logic gates covered in this course are:


AND

 Expression operator	Circuit symbol	Explanation
(A AND B)		Returns TRUE only if both inputs are TRUE TRUE AND TRUE = TRUE Otherwise = FALSE


OR

 Expression operator	Circuit symbol	Explanation
(A OR B)		Returns TRUE if either input is TRUE TRUE OR FALSE = TRUE FALSE OR FALSE = FALSE


NOT

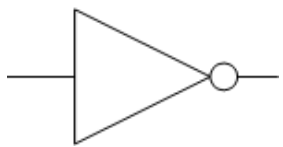Expression operator	Circuit symbol	Explanation
(NOT A)		Reverses the input value NOT TRUE = FALSE NOT FALSE = TRUE


XOR (exclusive OR)

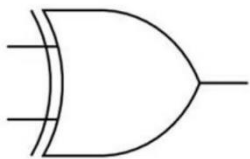Expression operator	Circuit symbol	Explanation
(A XOR B)		Returns TRUE if either input is TRUE but NOT both TRUE OR FALSE = TRUE FALSE OR FALSE = FALSE TRUE OR TRUE = FALSE

NAND (not AND)

 Expression operator	Circuit symbol	Explanation
(A NAND B)		Returns TRUE if either or both inputs are FALSE TRUE OR FALSE = TRUE FALSE OR FALSE = TRUE TRUE OR TRUE = FALSE

NOR (not OR)

 Expression operator	Circuit symbol	Explanation
(A NOR B)		Returns TRUE if both inputs are FALSE TRUE OR FALSE = FALSE FALSE OR FALSE = TRUE TRUE OR TRUE = FALSE




Examiner Tips and Tricks

You will need to either draw a diagram of a logic circuit using these symbols, or you will have to write the boolean expression from an existing diagram.

Logic Circuits


What is a logic circuit?

- A logic circuit **performs logical operations** on binary information
- Logic gates are **core components** of logic circuits
- Based on the **arrangement of logic gates** and the **input signals**, the circuit performs a specific function
- A logic diagram is a **visual representation** of combinations of logic gates within a logic circuit
- **Brackets** are used to clarify the **order** of operations
- An example logic diagram for the Boolean expression $Q = \text{NOT}(A \text{ OR } B)$ would be:

 

- In the logic diagram above, the **inputs** are represented by **A and B**
- **P** is the **output** of the OR gate on the left and becomes the input of the NOT gate
- **Q** is the **final output** of the logic circuit

Example of combining logic gates

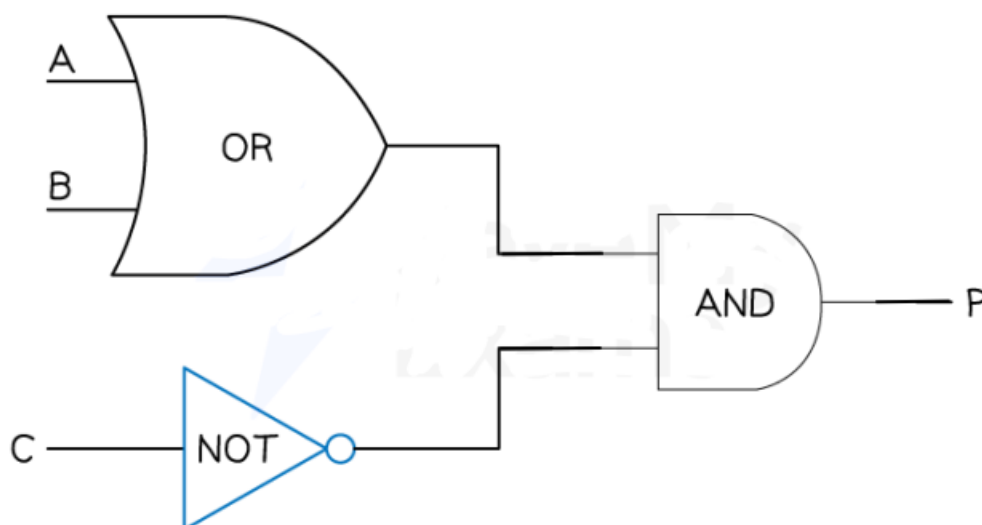


$$P = (A \text{ OR } B) \text{ AND NOT } C$$

Worked Example

A sprinkler system switches on if it is not daytime (input A) and the temperature is greater than 40 (input B)


Draw a logic circuit to represent the problem statement above [2]


Answers

 



Truth Tables


- A truth table is a tool used in logic and computer science to **visualise the results of Boolean expressions**
- They represent **all possible inputs** and the **associated outputs** for a **given Boolean expression**

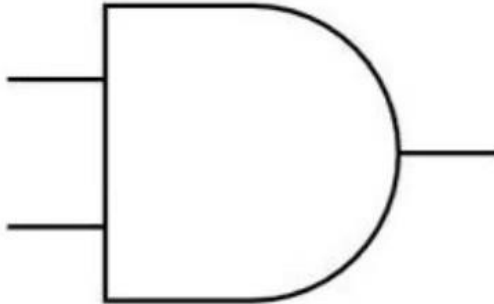
AND		
Circuit symbol	Truth Table	
		

 OR																	
Circuit symbol	Truth Table																
	<table><tr><th colspan="2">INPUTS</th><th>OUTPUTS</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>		INPUTS		OUTPUTS	0	0	0	0	1	1	1	0	1	1	1	1
INPUTS		OUTPUTS															
0	0	0															
0	1	1															
1	0	1															
1	1	1															

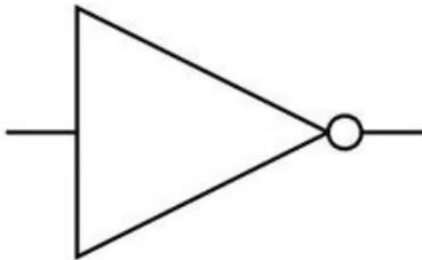NOT								
Circuit symbol		Truth Table						
		<table><tr><th>INPUTS</th><th>OUTPUTS</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	INPUTS	OUTPUTS	0	1	1	0
INPUTS	OUTPUTS							
0	1							
1	0							

 XOR (exclusive)																	
Circuit symbol	Truth Table																
	<table><tr><th colspan="2">INPUTS</th><th>OUTPUTS</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>		INPUTS		OUTPUTS	0	0	0	0	1	1	1	0	1	1	1	0
INPUTS		OUTPUTS															
0	0	0															
0	1	1															
1	0	1															
1	1	0															

 NAND (Not AND)																	
Circuit symbol	Truth Table																
	<table><tr><th colspan="2">INPUTS</th><th>OUTPUTS</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>		INPUTS		OUTPUTS	0	0	1	0	1	1	1	0	1	1	1	0
INPUTS		OUTPUTS															
0	0	1															
0	1	1															
1	0	1															
1	1	0															

 
NOR (Not OR)																	
Circuit symbol	Truth Table																
	<table><tr><th colspan="2">INPUTS</th><th>OUTPUTS</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>		INPUTS		OUTPUTS	0	0	1	0	1	0	1	0	0	1	1	0
INPUTS		OUTPUTS															
0	0	1															
0	1	0															
1	0	0															
1	1	0															


How do you create truth tables for logic circuits?


- To create a truth table for the expression **P = (A AND B) AND NOT C**
 - Calculate the numbers of rows needed (**2^{number of inputs}**)
 - In this example there are 3 inputs (**A, B, C**) so a total of **8 rows** are needed (**2³**)
 - To not miss any combination of inputs, start with **000** and **count** up in **3-bit binary (0–7)**


Logic Expressions


- A **logic expression** is a way of expressing a logic gate or logic circuit as an **equation**
- The **output** appears on the **left** of the equals sign with the **inputs** and **logic gates** on the **right**

 
AND				
Circuit symbol	Truth Table			Logic Expression
	INPUTS		OUTPUTS	Z = A AND B
	A	B	Z	
	0	0	0	
	0	1	0	
	1	0	0	
	1	1	1	

 OR				
Circuit symbol	Truth Table			Logic Expression
	INPUTS		OUTPUTS	Z = A OR B
	A	B	Z	
	0	0	0	
	0	1	1	
	1	0	1	
	1	1	1	

 
NOT														
Circuit symbol	Truth Table	Logic Expression												
	<table border="1"> <thead> <tr> <th colspan="2">INPUTS</th><th>OUTPUTS</th></tr> <tr> <th>A</th><th></th><th>Z</th></tr> </thead> <tbody> <tr> <td>0</td><td></td><td>1</td></tr> <tr> <td>1</td><td></td><td>0</td></tr> </tbody> </table>	INPUTS		OUTPUTS	A		Z	0		1	1		0	$Z = \text{NOT } A$
INPUTS		OUTPUTS												
A		Z												
0		1												
1		0												

 NAND																				
Circuit symbol	Truth Table	Logic Expression																		
	<table border="1"> <thead> <tr> <th colspan="2">INPUTS</th><th>OUTPUT</th></tr> <tr> <th>A</th><th>B</th><th>Z</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	INPUTS		OUTPUT	A	B	Z	0	0	1	0	1	1	1	0	1	1	1	0	$Z = A \text{ NAND } B$
INPUTS		OUTPUT																		
A	B	Z																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		

 NOR																				
Circuit symbol	Truth Table	Logic Expression																		
	<table border="1"> <thead> <tr> <th colspan="2">INPUTS</th><th>OUTPUT</th></tr> <tr> <th>A</th><th>B</th><th>Z</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	INPUTS		OUTPUT	A	B	Z	0	0	1	0	1	0	1	0	0	1	1	0	$Z = A \text{ NOR } B$
INPUTS		OUTPUT																		
A	B	Z																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	0																		

 XOR (Exclusive OR)																					
Circuit symbol	Truth Table		Logic Expression																		
	<table><tr><th colspan="2">INPUTS</th><th>OUTPUT</th></tr><tr><th>A</th><th>B</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>		INPUTS		OUTPUT	A	B	Z	0	0	0	0	1	1	1	0	1	1	1	0	Z = A XOR B
	INPUTS		OUTPUT																		
	A	B	Z																		
	0	0	0																		
	0	1	1																		
	1	0	1																		
	1	1	0																		

From a circuit, build a Truth Table

 

Steps:

- Identify all the possible **combinations of input**
- Work out the solution for **intermediate output** (layer by layer)
- Using the intermediate outputs, construct the **final output**

Step 1:


Identify all the possible combinations of input (we have 3 inputs)

$$2^3 = 8 \text{ rows}$$

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Step 2:


Identify the intermediate outputs. Solve them one by one.

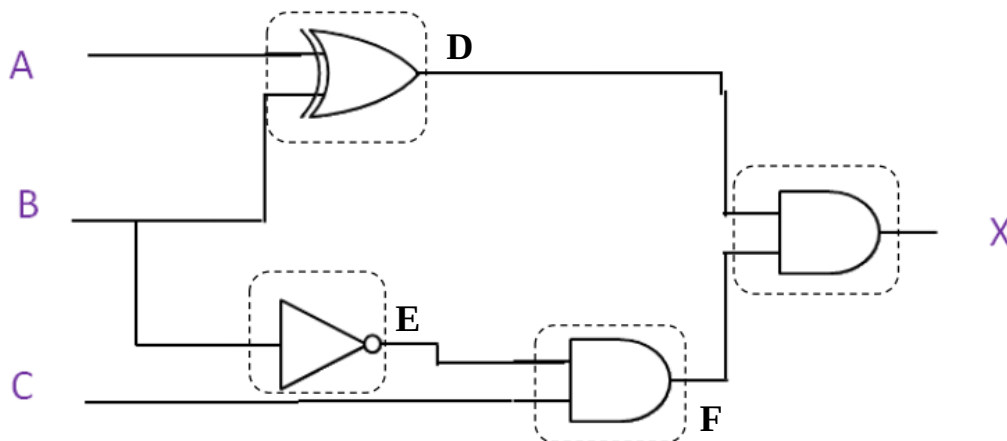**Step 3:**

Using the intermediate outputs, construct the final output.


A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 From a circuit, build a logical expression



Step 1:

 Look at the gates connected to A, B and C.



Step 2:

Then, form an expression with gate 1, gate 2 and gate 3.

Gate 1 = A XOR B

Gate 2 = NOT B

Gate 3 = Gate 2 AND C

↓ Substitution

Gate 3 = NOT B AND C

Step 3:

Then, form an expression with FINAL gate 4.

Gate 4 = Gate 1 AND Gate 3

Substitution

Gate 4 = (A XOR B) AND (NOT B AND C)

Final logical expression

X = (A XOR B) AND (NOT B AND C)

From a logical expression, build a circuit

$$X = (A \text{ NAND } C) \text{ XOR } (\text{NOT } B \text{ OR } C)$$

To solve this problem, we need to **break down** the statement into smaller pieces.


Part 1: (A NAND C)

Part 2: (NOT B OR C)


Part 3: (Part 1) XOR (Part 2)

Let's build the circuit piece by piece


Part 1: (A NAND C)

 

Part 2: (NOT B OR C)

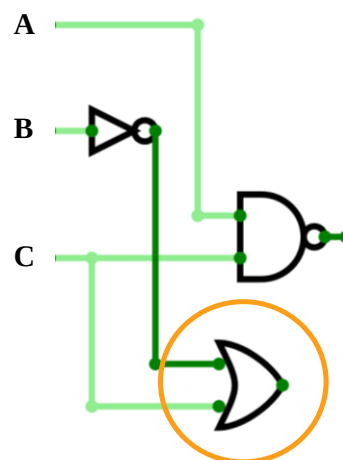

Part 3: (Part 1) XOR (Part 2)

 

From a truth table, build a logical expression and a circuit

INPUT		OUTPUT
A	B	X
0	0	0
0	1	0
1	0	1
1	1	0

Steps to follow to build logical expression

1. To produce the logical expression, look at only the row where the **output value is 1**
2. Combine each input with an **AND** statement
3. If the input value is **zero**, negate it using **NOT** gate

Negate B (which is 0)

$X = A \text{ AND } (\text{NOT } B)$

Combine each input

If more than one row have output value 1.

1. Follow the **above steps** and create logical expression for **each row separately**
2. **Concatenate** these statements with **OR** gate

For example:

INPUT		OUTPUT
A	B	X
0	0	0
0	1	1
1	0	0
1	1	1

1st row: (NOT A) AND B

2nd row: A AND B

1st row **OR** 2nd row

↓ Substitution

$$X = ((\text{NOT } A) \text{ AND } B) \text{ OR } (A \text{ AND } B)$$

From a problem statement, draw a logic gate

(b) A water control system uses a switch and two pressure sensors.

The outputs of the switch and sensors are shown in the table.

Sensor or Switch	Output of 1	Output of 0
Switch (S1)	On	Off
Pressure Sensor (P1)	≥ 3	< 3
Pressure Sensor (P2)	≥ 3	< 3

Create a logic circuit that will produce an output (X) of 1 when:

The switch S1 is on

and

either P1 is less than 3 or P2 is less than 3, but not both.

Simplifying the problem statement

S1 AND (NOT P1 XOR NOT P2)

- Understand the problem first
- Identify the **inputs** (in this problem we have 3 inputs. S1, P1 and P2)
- Look for the **keywords**. For example **and**, **or**
- If any output is **zero**, then need to make a **NOT gate**

Sensor or Switch	Output of 1	Output of 0
Switch (S1)	On	Off
Pressure Sensor (P1)	≥ 3	< 3
Pressure Sensor (P2)	≥ 3	< 3

Output is 0 for this both value. That is why used NOT gate

Create a logic circuit that will produce an output (X) of 1 when:

The switch S1 is on

and

either P1 is less than 3 or P2 is less than 3 but not both.

S1 AND (NOT P1 XOR NOT P2)

Why not OR gate?

either P1 is less than 3 or P2 is less than 3, but not both.

Read the statement carefully. It says not both.

XOR gate only gives output 1 if only one input is 1.

INPUTS		OUTPUT
A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0